



# AN781: Alternative Output Termination for Si5211x, Si5213x, Si5214x, Si5216x, Si522xx, Si5310x, Si5311x, and Si5315x PCIe Clock Generator and Buffer Families

---

This application note is intended to provide optional, alternative output terminations for converting a low-power HCSL output clock from a Silicon Labs PCIe clock generator or buffer device into a LVPECL, LVDS, or CML formatted clock. These optional terminations are particularly useful in applications that require both 100 MHz PCIe output clocks, as well as 100 MHz LVDS, LVPECL, or CML output clocks for FPGAs, SGMII, or other chipsets. Rather than using separate clock generators or oscillators to satisfy these system requirements, one can utilize a single-clock generator or buffer IC from Silicon Labs and employ different terminations on each output to achieve the desired results. It is relevant to note all Silicon Labs devices that provide HCSL PCIe outputs utilize low-power, push-pull buffers as opposed to constant current mode buffers. There are many advantages to using low-power, push-pull output buffers, including lower power consumption, elimination of external termination resistors, and overall reduction in total PCB area.

#### KEY FEATURES OR KEY POINTS

---

- Translate HCSL to LVPECL, LVDS or CML levels
- Reduce Power Consumption
- Simplify BOM AVL

## 1. Conversion of HCSL Signals to LVPECL Signals

A low-power, push-pull HCSL output clock can be converted to either 2.5 V or 3.3 V LVPECL standards by using an output termination as shown in Figure 1.1 Termination Scheme for HCSL to LVPECL Conversion on page 2. Figure 1.2 Oscilloscope Measurement of LVPECL Conversion on page 2 shows the output clock at the measurement point indicated in Figure 1.1 Termination Scheme for HCSL to LVPECL Conversion on page 2. VCC supply is required to set the common mode voltage at the receiver end. Table 1.1 Resistor Selection for Different VCC Standards (LVPECL Signal Conversion) on page 3 lists the resistor selection based on VCC.

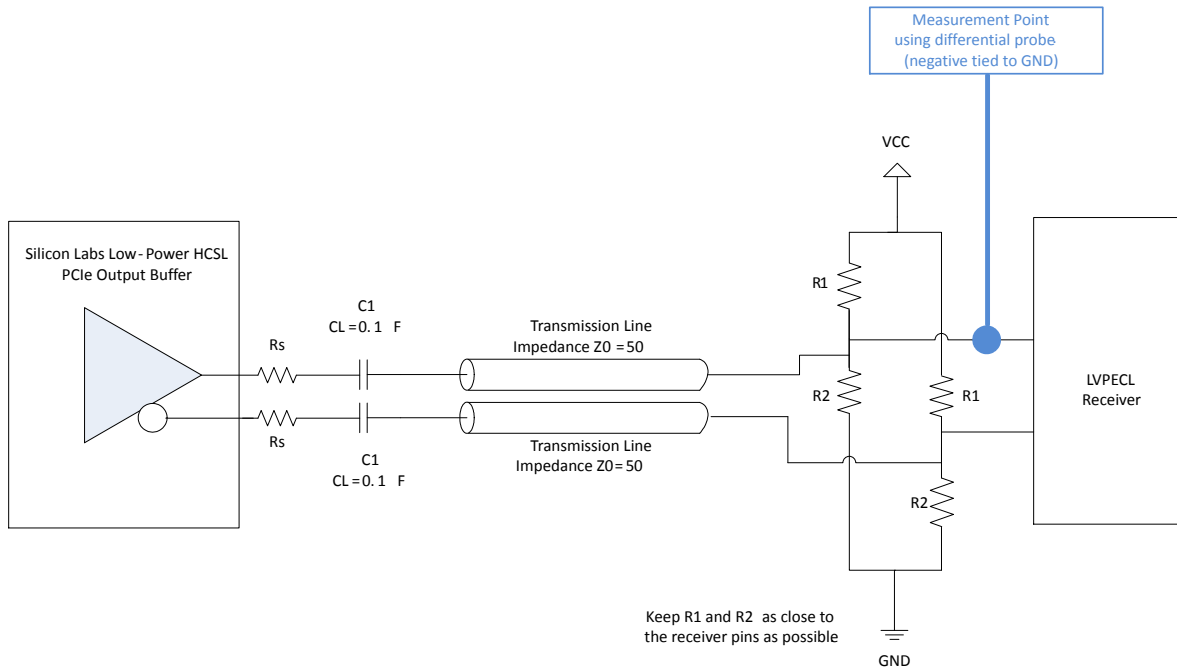


Figure 1.1. Termination Scheme for HCSL to LVPECL Conversion

 


Figure 1.2. Oscilloscope Measurement of LVPECL Conversion

**Table 1.1. Resistor Selection for Different VCC Standards (LVPECL Signal Conversion)**

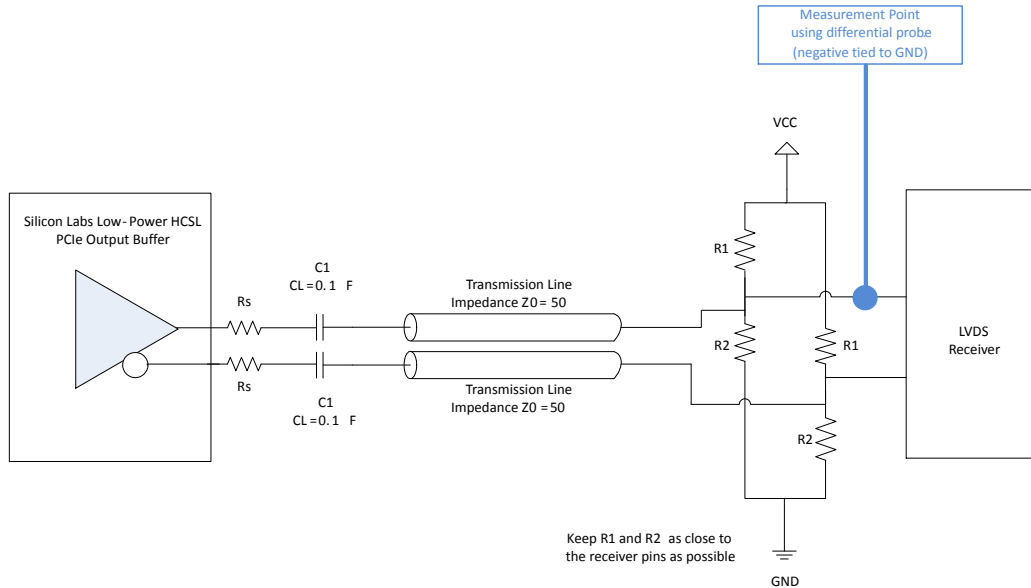
VCC	Expected Common Mode Voltage (V)	R1 (kΩ)	R2 (kΩ)
3.3	2	3	5
2.5	1.1	5	4

**Table 1.2. Series Resistor Selection for PCIe Clock Generators and Buffers**

Device	Zdiff (Ω)	Rs (Ω)
Si5310x, Si5311x	100	33
Si5211x, Si5213x, Si5214x, Si5216x, Si5315x	100	0
Si52202/04/08/12	100	0

## 2. Conversion of HCSL Signals to LVDS Signals

One can also convert a low-power, push-pull HCSL clock output to a 1.8 V, 2.5 V, or 3.3 V LVDS clock output. The recommended termination scheme is shown in [Figure 2.1 Termination Scheme for Low-Power HCSL to LVDS Conversion \(When Receiver has no Termination or Internal 100 Ω Termination\)](#) on page 4, with the corresponding oscilloscope measurement shown in [Figure 2.2 Oscilloscope Measurement of LVDS Conversion \(When Receiver has no Internal Termination\)](#) on page 4 (at the measurement point indicated in [Figure 2.1 Termination Scheme for Low-Power HCSL to LVDS Conversion \(When Receiver has no Termination or Internal 100 Ω Termination\)](#) on page 4).

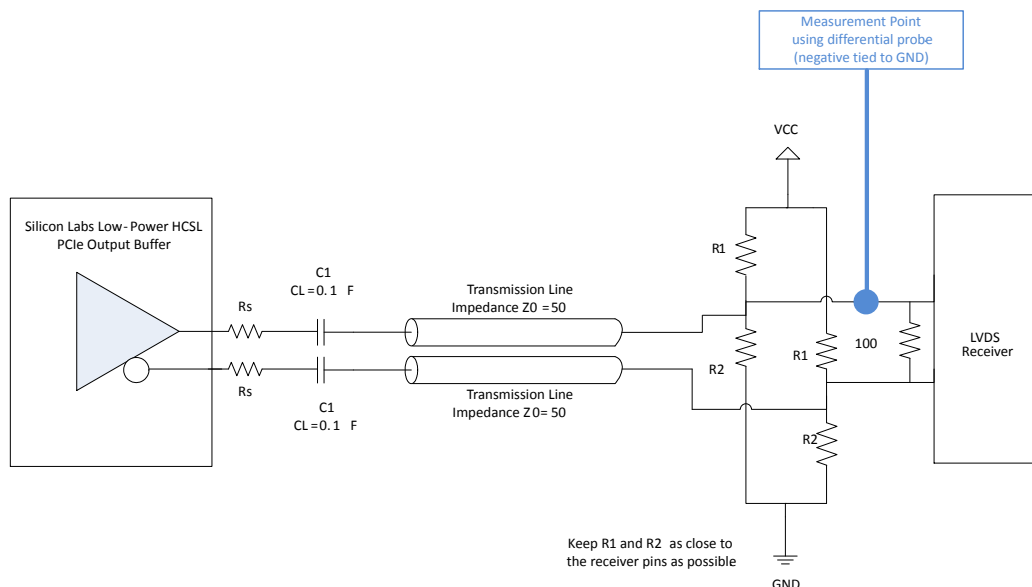


**Figure 2.1. Termination Scheme for Low-Power HCSL to LVDS Conversion (When Receiver has no Termination or Internal 100 Ω Termination)**

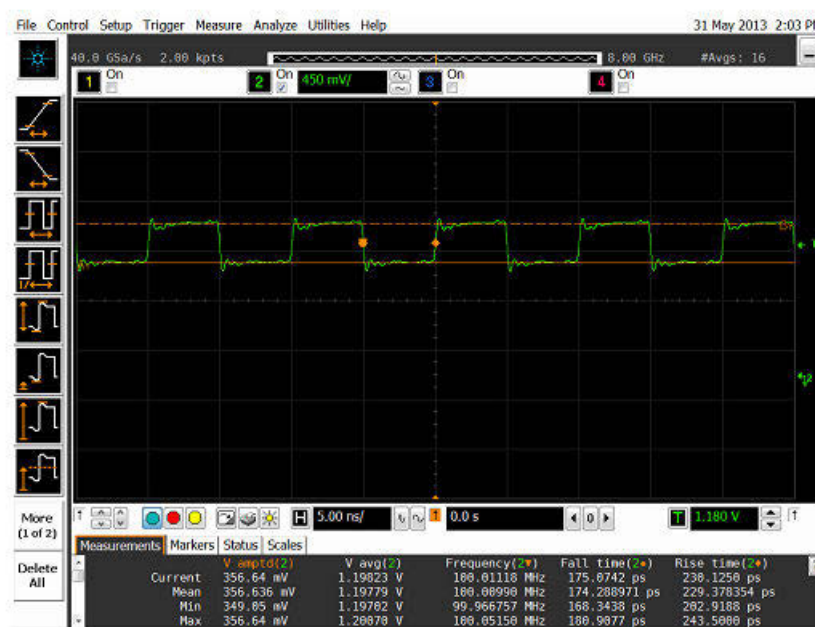


**Figure 2.2. Oscilloscope Measurement of LVDS Conversion (When Receiver has no Internal Termination)**

The swing will be reduced by 50% by an internal or external termination (the signal will be similar to the signal seen in [Figure 2.4 Oscilloscope Measurement of LVDS Conversion \(When Receiver has Internal or External 100 Ω Termination\)](#) on page 5). If the receiver does not have an internal 100 Ω termination, an external 100 Ω termination may be added, as shown in [Figure 2.3 Termination Scheme for Low-Power HCSL to LVDS Conversion \(When Receiver has no Internal 100 Ω Termination\)](#) on page 5.



**Figure 2.3. Termination Scheme for Low-Power HCSL to LVDS Conversion (When Receiver has no Internal 100  $\Omega$  Termination)**



**Figure 2.4. Oscilloscope Measurement of LVDS Conversion (When Receiver has Internal or External 100  $\Omega$  Termination)**

The resistor selection guide for different VCC values at the receiver end is given in [Table 2.1 Resistor Selection on page 5](#).


**Table 2.1. Resistor Selection**

Voltage Standard (V)	Expected Common Mode Voltage (V)	R1 (k $\Omega$ )	R2 (k $\Omega$ )
3.3	1.2	5	2.85
2.5	1.2	6	5.5
1.8	1.2	3	6


For series resistor selection of PCIe clock generators and buffers, see [Table 1.2 Series Resistor Selection for PCIe Clock Generators and Buffers on page 3](#).

### 3. Conversion of HCSL Signals to CML Signals (AC Coupled to Receivers)

AC coupling is the recommended method for converting low-power HCSL signals to CML. The receiver should be able to generate the references needed to generate the common mode for CML signals. The recommended schematic is shown in [Figure 3.1 Termination Scheme for HCSL to CML AC Coupling on page 6](#). It is also important to note that many CML receivers come with internal 50  $\Omega$  terminations to VCC, as shown in [Figure 3.2 Typical CML Receiver Circuit Structure on page 6](#). Such internal terminations can reduce the signal swing by 50%.

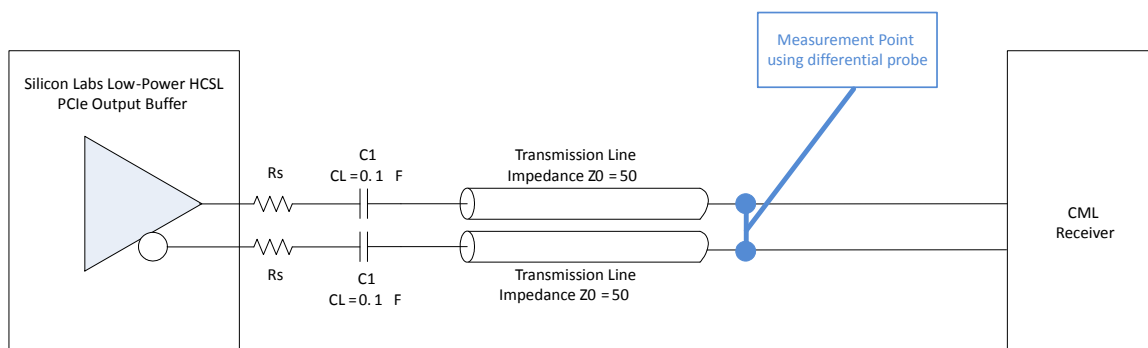

**Figure 3.1. Termination Scheme for HCSL to CML AC Coupling**

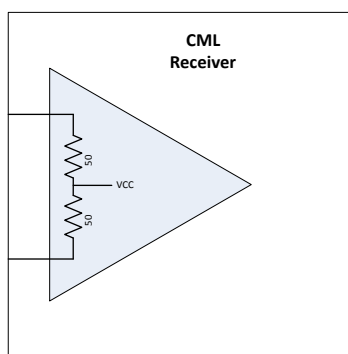


**Figure 3.2. Typical CML Receiver Circuit Structure**

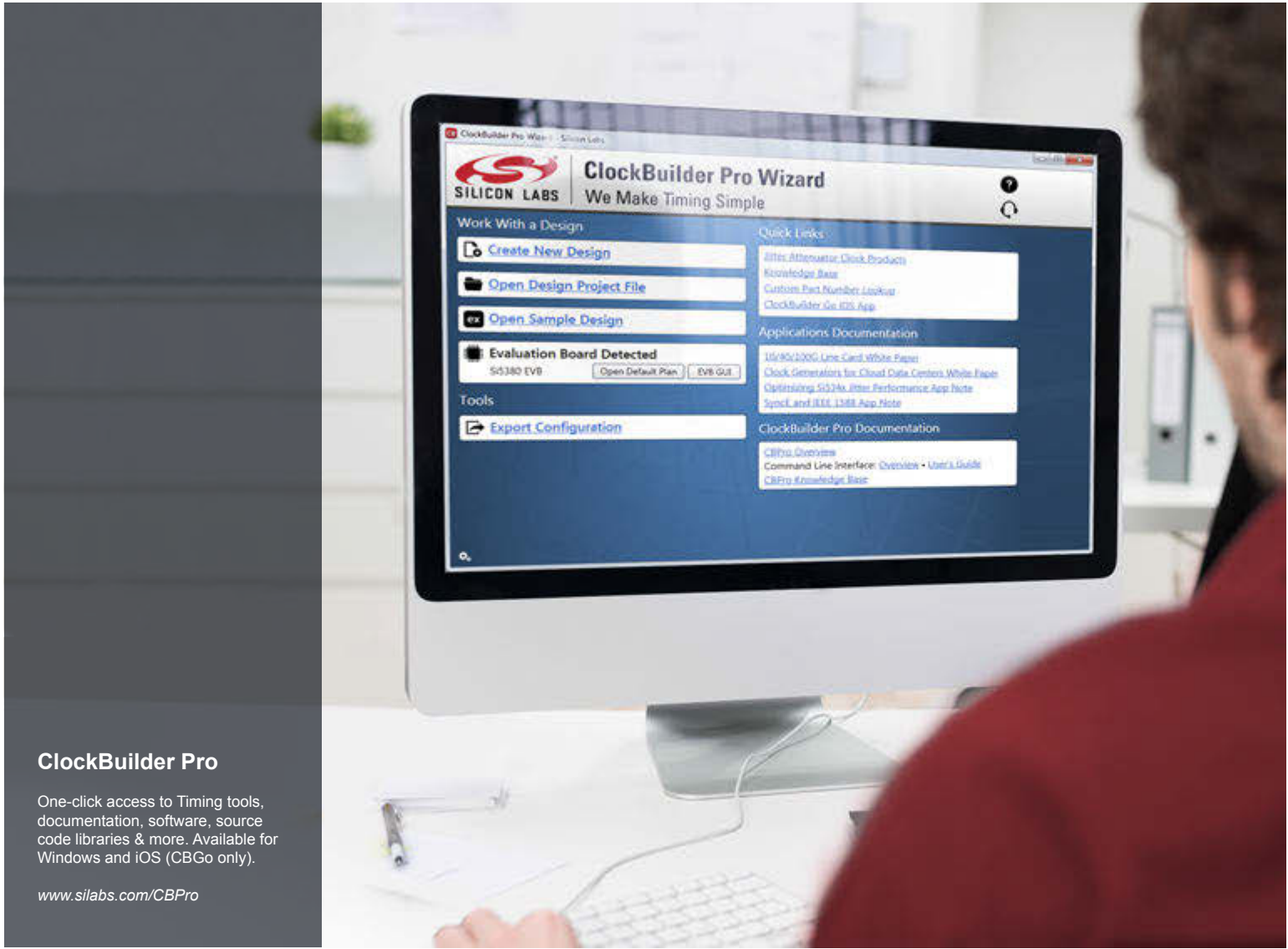---

## 4. Conclusion

This application note details methods in which low-power HCSL output clocks from the Si5211x, Si5213x, Si5214x, Si5216x, Si5310x, Si5311x, Si5315x, and Si522xx device families can be used to drive receivers that use other differential formats, specifically LVPECL, LVDS, and CML standards.



## ClockBuilder Pro

One-click access to Timing tools, documentation, software, source code libraries & more. Available for Windows and iOS (CBGo only).

[www.silabs.com/CBPro](http://www.silabs.com/CBPro)



**Timing Portfolio**  
[www.silabs.com/timing](http://www.silabs.com/timing)



**SW/HW**  
[www.silabs.com/CBPro](http://www.silabs.com/CBPro)



**Quality**  
[www.silabs.com/quality](http://www.silabs.com/quality)



**Support and Community**  
[community.silabs.com](http://community.silabs.com)

### Disclaimer

Silicon Labs intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Labs products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Labs reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Labs shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products are not designed or authorized to be used within any Life Support System without the specific written consent of Silicon Labs. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Labs products are not designed or authorized for military applications. Silicon Labs products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

### Trademark Information

Silicon Laboratories Inc.®, Silicon Laboratories®, Silicon Labs®, SiLabs® and the Silicon Labs logo®, Bluegiga®, Bluegiga Logo®, Clockbuilder®, CMEMS®, DSPLL®, EFM®, EFM32®, EFR, Ember®, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZRadio®, EZRadioPRO®, Gecko®, ISOModem®, Micrium, Precision32®, ProSLIC®, Simplicity Studio®, SiPHY®, Telegesis, the Telegesis Logo®, USBXpress®, Zentri and others are trademarks or registered trademarks of Silicon Labs. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



**Silicon Laboratories Inc.**  
400 West Cesar Chavez  
Austin, TX 78701